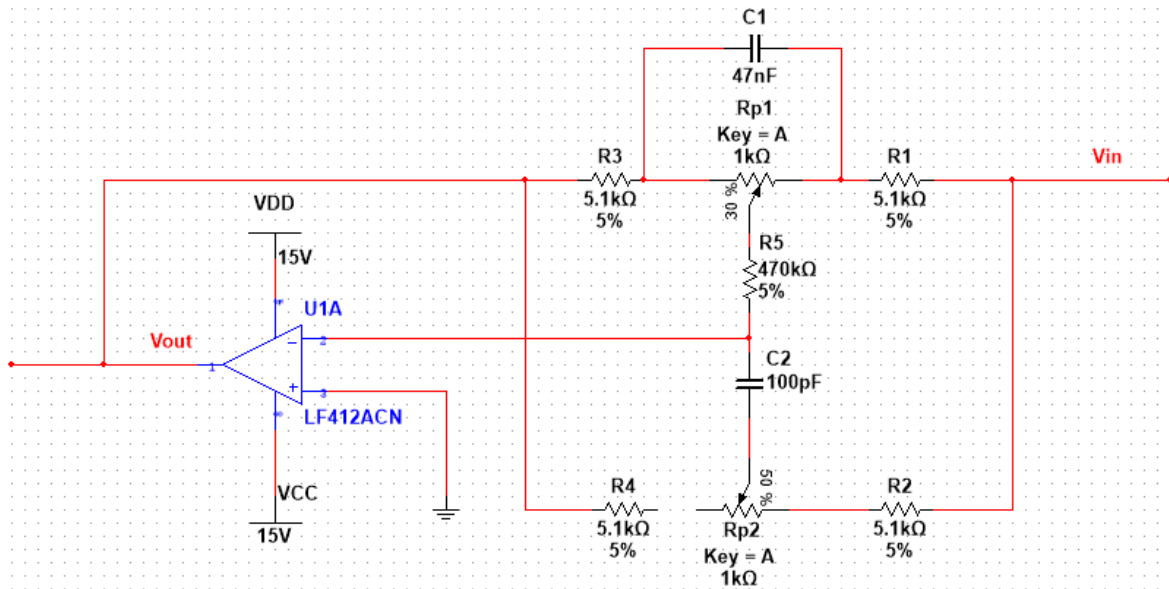


For R_f , i use 8.2k to replace it.


$$-V_{out} = -(0.5 + 0.5) = -1V$$

$$V_{out \text{ max}} = 1V, V_{out \text{ min}} = 0V$$

According to the function, $(V_{out} - V_{in}) / (5.1k + 5.1k + R_{p2}) = (V_{in} - V_{out}) / (5.1k + 5.1k + R_{p1})$
 $V_{out} / V_{in} = 1$, so gain of the circuit = 1 which is meet the requirement



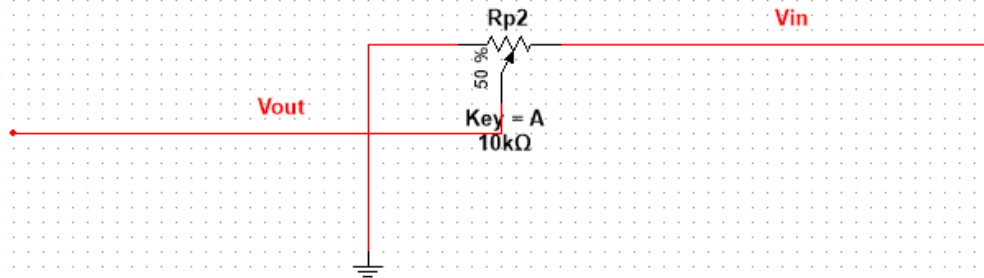we only have the 10k potentiometer, so this is our only choose



base on the solve the equation, for voltage division,
the ratio for R1-R5 is 52.4:2.1:1
however, i dont have enough resistor, i replace
2.2k->2k
3.9k->4k
47k->52k

